

Exercise

Please hand in this paper to the instructor before the end of the lecture.

Name: _____

Student number: _____ Date: _____

Q1. Implement the following sum-of-products expression using NOT, AND, and OR gates:

$$f(x, y, z) = x'yz' + xy'z.$$

Q2. Now implement the same method using only NAND gates.