

Basic Electronics

CSCI 2050U - Computer Architecture

Randy J. Fortier
[@randy_fortier](https://twitter.com/randy_fortier)

Lecture Outline

- Basic physics and electronics components
- Digital logic gates

Background

CSCI 2050U - Computer Architecture


Mechanical Computers

- Charles Babbage (1791-1871)
 - Difference engine (~1822)
 - Calculating astronomical tables
 - Analytical engine (never completed)
 - Programmable





Electromechanical Computers

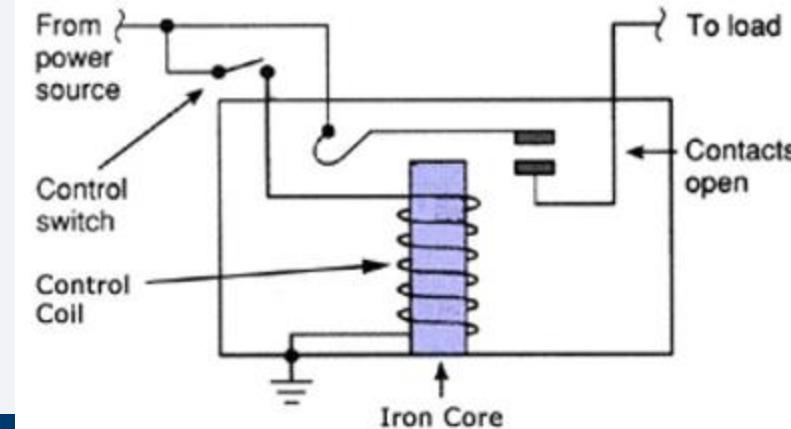- A relay is an electromechanical device which acts like a switch
 - Conceived by telegraph operators to relay (forward) a signal
 - The incoming data creates a new signal with the same output



Electromechanical Computers

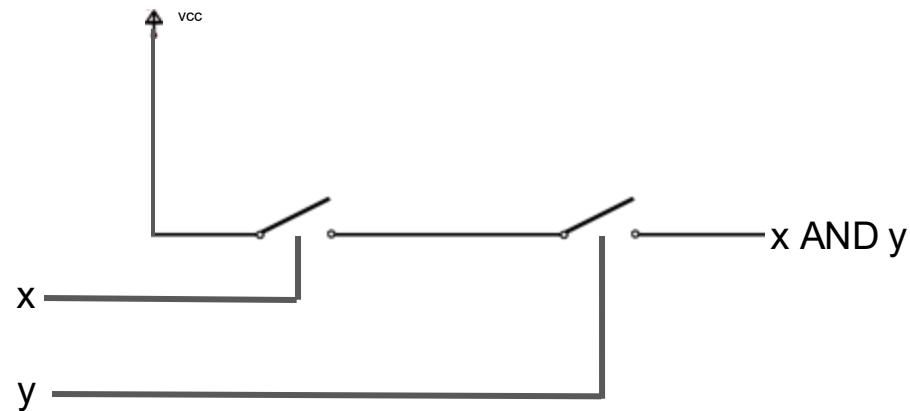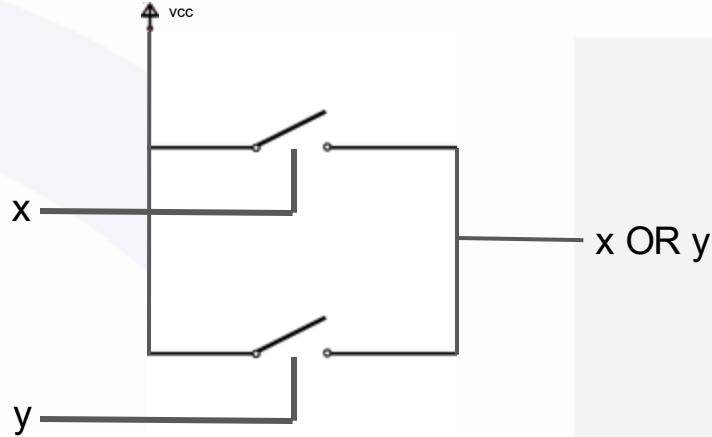- Imagine two relays, configured as in these diagrams:




Electromechanical Computers

- In theory, we could build a computer out of relays
 - It would be huge
 - It would use a lot of power
 - It would be expensive
 - It would break down a lot
- Computers like these were created by Harvard, Bell
 - 1940s - 1950s
- Alan Turing used a computer like this to crack the Enigma code in WWII

Electronics - Diodes and LEDs

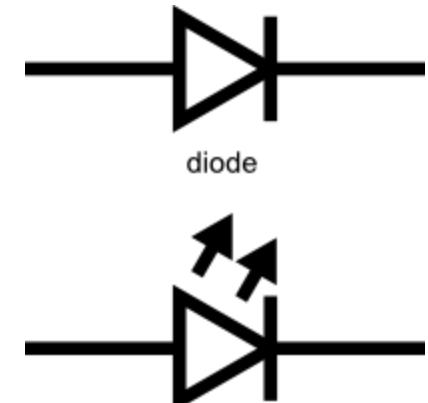- Some basic electronics terminology:
 - Diode: A device that forces flow in one direction
 - Anode: Electrons flow out (+)
 - Cathode: Electrons flow in (-)
 - Light Emitting Diode (LED): A diode that produces light




Electronics - Resistors

- Some basic electronics terminology:
 - Resistance: The degree to which a material resists electron flow
 - Analogy: A narrow pipe
 - Measured in Ohms (Ω)
 - Conductor: A material with low resistance (e.g. gold, copper)
 - Insulator: A material with high resistance (e.g. glass, rubber)
 - Semiconductor: A material whose resistance can be modified (called doping)
 - e.g. silicon, germanium



Ohm's Law

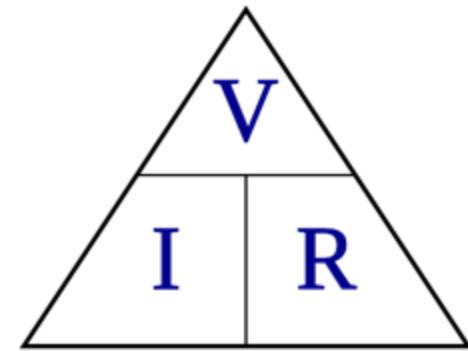- Voltage
 - A measure of pressure
 - Unit: volts
 - Can be negative or positive (direction of pressure)
 - Handy for encoding (discussed later)
- Current
 - A measure of flow
 - Unit: Amperes
- Wattage
 - A measure of work
 - Unit: watts



Ohm's Law:

$$V = IR$$

$$I = V/R$$

$$R = V/I$$

Electrical Computers - Vacuum Tubes

- Alternatives to relays:
 - Vacuum tubes
 - Low pressure tubes with anode and a heated cathode
 - Photoelectric effect causes electrons to flow only in one direction
 - ENIAC, Colossus
 - Expensive, energy waste, often fail
 - Transistors



Electrical Computers - Transistors

- Alternatives to relays:
 - Vacuum tubes
 - Transistors
 - Devices made in silicon
 - Developed in the 1950s and 1960s
 - Popularized in the 1970s
 - Energy efficient, small, rarely break down
 - Primary component of very large scale integration (VLSI) circuits



Electrical Computers

- Chemistry review:
 - Atoms can share electrons in their outermost shells (co-valent bonds)
 - Pure silicon crystal has 4/8 electrons in its outer shell, so it can bond with 4 other silicon atoms

Electrical Computers

- Chemistry review:
 - Atoms can share electrons in their outermost shells (co-valent bonds)
 - Pure silicon crystal has 4/8 electrons in its outer shell, so it can bond with 4 other silicon atoms
 - Silicon can be 'doped'
 - Phosphorus - has 5 electrons in its outer shell (one extra electron; N-type)

A standard periodic table of elements is displayed, showing the elements arranged in groups and periods. The table includes element symbols, atomic numbers, and some physical properties. The elements are color-coded into groups: alkali metals (Group 1), alkali earth metals (Group 2), transition metals (Groups 3-12), post-transition metals (Groups 13-18), and noble gases (Group 18). The table also includes the lanthanide and actinide series.

Group	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16	17	18
1	H																	He
2	Li	Be																Ne
3	Na	Mg																Ar
4	K	Ca	Sc															
5	Rb	Sr	Y															
6	Cs	Ba	La															
7	Fr	Ra	Ac															
8																		
9																		
10																		
11																		
12																		
13																		
14																		
15																		
16																		
17																		
18																		


Electrical Computers

- Chemistry review:
 - Atoms can share electrons in their outermost shells (co-valent bonds)
 - Pure silicon crystal has 4/8 electrons in its outer shell, so it can bond with 4 other silicon atoms
 - Silicon can be 'doped'
 - Phosphorus - has 5 electrons in its outer shell (one extra electron; N-type)
 - Boron - has 3 electrons in its outer shell (one extra hole; P-type)


Electrical Computers

- Diodes
 - A component that restricts the flow of electrons to a single direction
- How do they work?
 - Place an N-type semiconductor adjacent to a P-type semiconductor
 - The extra electrons in the N-type semiconductor occupy the holes in the P-type semiconductor for a small space near the junction (depletion zone)


Electrical Computers - Diodes

 

Electrical Computers - Diodes

 

Electrical Computers - Diodes

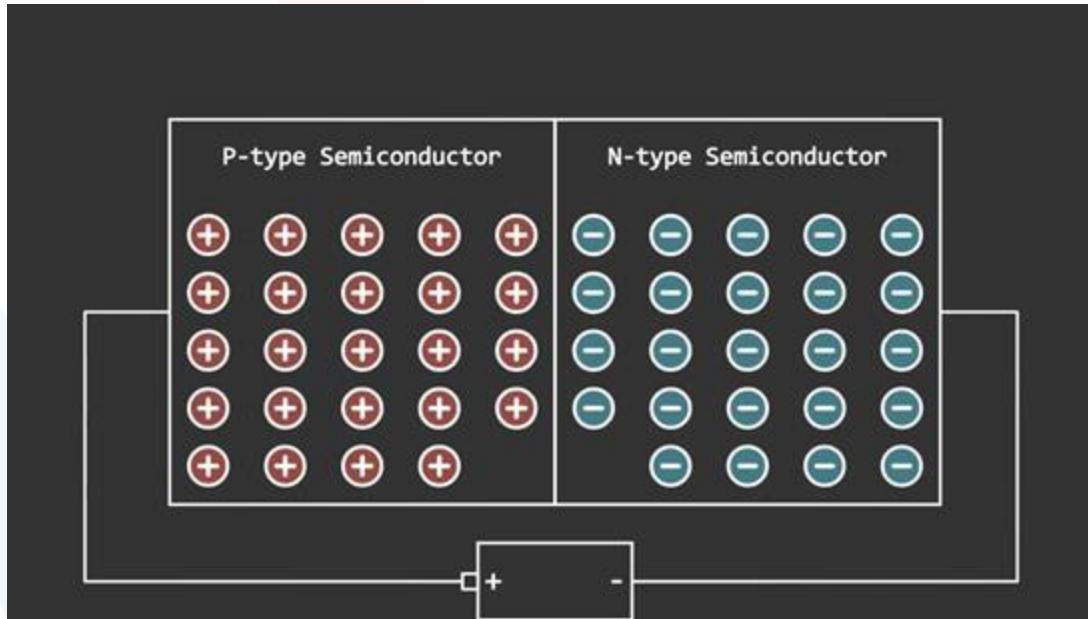


Electrical Computers - Transistors



Analog vs. Digital

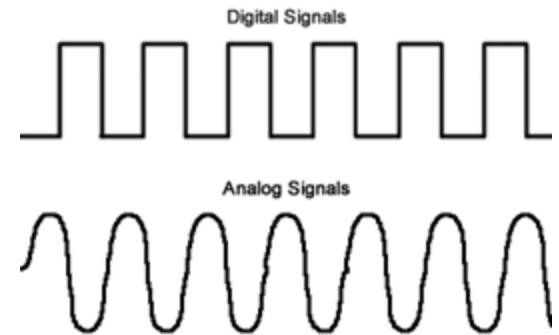- Digital
 - Represent only discrete values
 - e.g. 0-10% of the population voted → +0.5v
- Analog
 - Represent any continuous value
 - e.g. 71.3% of the population voted → +0.713v




Digital Logic Gates

CSCI 2050U - Computer Architecture

Basic Circuit Diagrams

- Inverter:

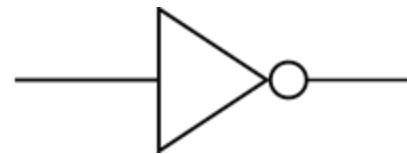


A	$NOT\ A\ (A')$
0	1
1	0

Basic Circuit Diagrams

- AND:



<i>A</i>	<i>B</i>	<i>A AND B (AB)</i>
0	0	0
0	1	0
1	0	0
1	1	1

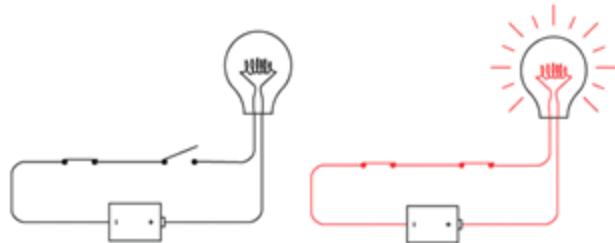

Basic Circuit Diagrams

- OR:


<i>A</i>	<i>B</i>	<i>A OR B (A+B)</i>
0	0	0
0	1	1
1	0	1
1	1	1

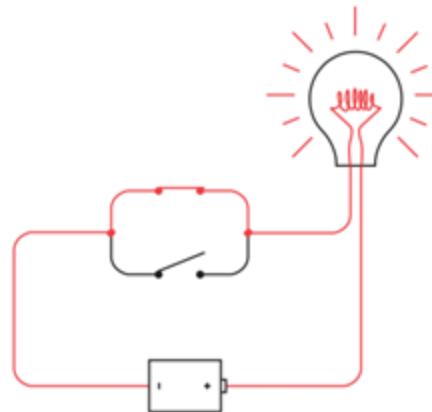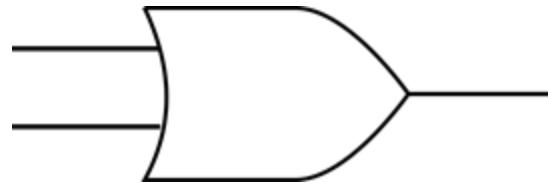

Basic Circuit Diagrams

- NOR:

<i>A</i>	<i>B</i>	<i>A NOR B</i>
0	0	1
0	1	0
1	0	0
1	1	0

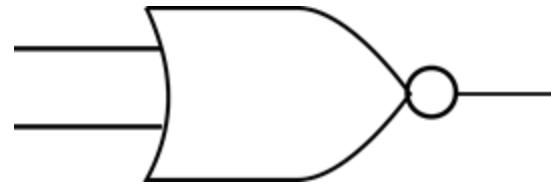

Basic Circuit Diagrams

- NAND:

<i>A</i>	<i>B</i>	<i>A NAND B</i>
0	0	1
0	1	1
1	0	1
1	1	0



Universal Gates

- NAND and NOR are both considered universal gates
 - Any circuit that can be built with AND, OR, and NOT can also be built exclusively with NAND gates (or NOR gates)


Universal Gates

- NAND and NOR are both considered universal gates
 - Any circuit that can be built with AND, OR, and NOT can also be built exclusively with NAND gates (or NOR gates)
- NOT:




Universal Gates

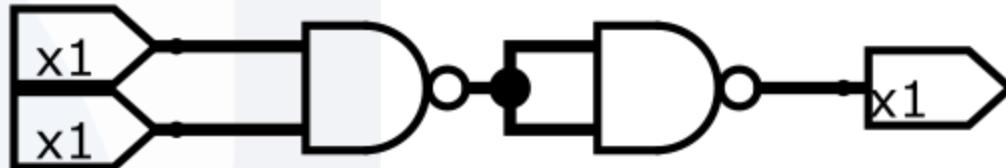- NAND and NOR are both considered universal gates
 - Any circuit that can be built with AND, OR, and NOT can also be built exclusively with NAND gates (or NOR gates)
- AND:



Universal Gates

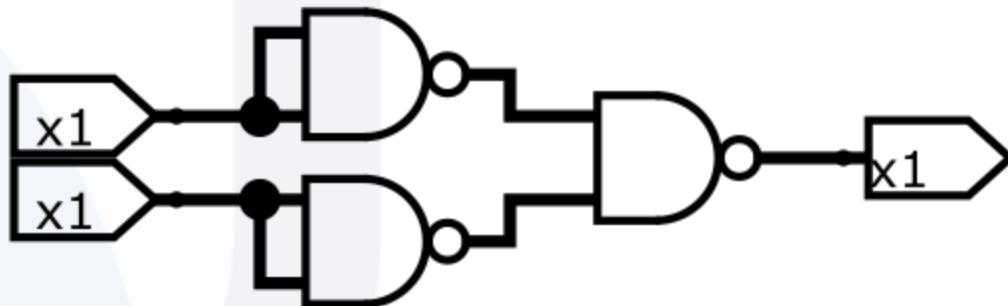- NAND and NOR are both considered universal gates
 - Any circuit that can be built with AND, OR, and NOT can also be built exclusively with NAND gates (or NOR gates)
- OR:



Homework

- Install the following digital circuit design package before our next lecture:
 - LogiSim Evolution - <https://github.com/reds-heig/logisim-evolution>
 - Instructions are provided on Canvas, under Assignments

Wrap-up

- Basic electronics
 - mechanical → electromechanical → electrical
 - relays → vacuum tubes → transistors
 - basic electronics
 - digital vs. analog
- Basic logic gates

What is next?

- Binary addition
- Half adder
- Full adder
- Ripple carry adder
- Fast carry adder