

Binary Arithmetic I

CSCI 2050U - Computer Architecture

Randy J. Fortier
@randy_fortier

Outline

- Binary addition
- Half adder
- Full adder
- Ripple carry adder
- Fast carry adder

Binary Addition

CSCI 2050U - Computer Architecture

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 1001 \ 0101 \\ + \underline{0001 \ 1100} \end{array}$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 1001 \ 010\mathbf{1} \\ + 0001 \ 110\mathbf{0} \\ \hline 1 \end{array} \quad (1+0=1)$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 1001 \ 0101 \\ + 0001 \ 1100 \\ \hline 01 \end{array} \quad (0+0=0)$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 1 \\ 1001 \ 0\mathbf{1}01 \\ + \ 0001 \ 1\mathbf{1}00 \\ \hline 001 \end{array} \quad (1+1=2, \text{ in binary } 2 \text{ is } 10)$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 1 \ 1 \\ 1001 \ 0101 \\ + \ 0001 \ \underline{1100} \\ \hline 0001 \end{array}$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} \mathbf{11} \quad 1 \\ 100\mathbf{1} \quad 0101 \\ + \quad \underline{000\mathbf{1} \quad 1100} \\ \mathbf{1} \quad 0001 \end{array} \quad (1+1+1=3, \text{ in binary } 3 \text{ is } 11)$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 11 \ 1 \\ 1001 \ 0101 \\ + \ 0001 \ 1100 \\ \hline 11 \ 0001 \end{array}$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 11 \ 1 \\ 1001 \ 0101 \\ + \ 0001 \ 1100 \\ \hline 011 \ 0001 \end{array}$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 11 \ 1 \\ 1001 \ 0101 \\ + \ 0001 \ 1100 \\ \hline 1011 \ 0001 \end{array}$$

Adding Binary Numbers

- Adding two binary numbers is very similar to adding two decimal numbers
 - Except that the digits cannot exceed 1 (unlike decimal, where 9 is the limit)

$$\begin{array}{r} 11 \ 1 \\ 1001 \ 0101 \quad 149 \\ + \ 0001 \ 1100 \quad +28 \\ \hline 1011 \ 0001 \quad 177 \end{array}$$

Adding Binary Numbers

- If there is a carry, because computers store data in finite spaces, we can't add any extra digits
 - There is no way to correctly encode the result
 - We have to throw away the carry, and the result will be wrong
 - This is called overflow

$$\begin{array}{r} 1 & 1 & 1 & 1 \\ 1001 & 0101 & & 149 \\ + & \underline{1001 \ 0101} & \underline{149} \\ 0010 & 1010 & & 42 \text{ (incorrect)} \end{array}$$

Adder Circuits

CSCI 2050U - Computer Architecture

Half Adder

- A half adder (HA) can add two bits together
 - Inputs:
 - A and B: The two bits to add
 - Outputs:
 - S: The sum of the two bits
 - C: Carry (1 if there was a carry, 0 if not)

Half Adder

- A half adder can add two bits together

A	B	S	C
0	0		
0	1		
1	0		
1	1		

Half Adder


- A half adder can add two bits together
 - [This](#) truth table is that of the XOR gate: $S = A'B + AB' = A \oplus B$

A	B	S	C
0	0	0	
0	1	1	
1	0	1	
1	1	0	

Exclusive OR

- XOR:

<i>A</i>	<i>B</i>	<i>A XOR B</i>
0	0	0
0	1	1
1	0	1
1	1	0

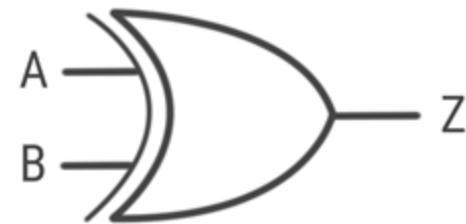

Half Adder


- A half adder can add two bits together
 - Recognize **this** truth table? $C = AB$

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Half Adder


- A half adder circuit:

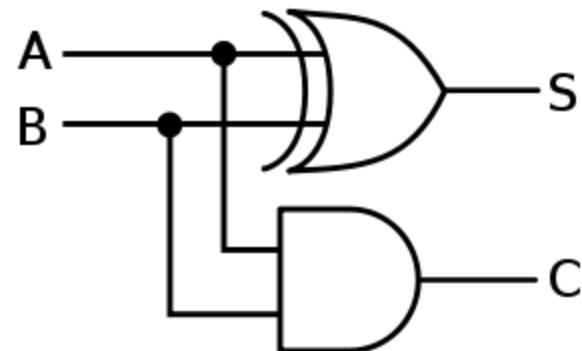- $S = A'B + AB' = A \oplus B$
- $C = AB$



Half Adder

- A half adder in block notation:

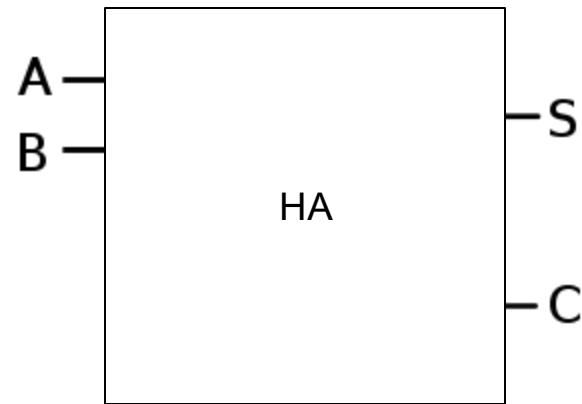

Full Adder

- Why do they call it a half adder?
- To find the answer to this, we need to try to add two multi-bit numbers
- Let's add 0011 and 0111:

$$\begin{array}{r} 0011 \\ +0111 \\ \hline \end{array}$$

Full Adder

- Why do they call it a half adder?
- To find the answer to this, we need to try to add two multi-bit numbers
- Let's add 0011 and 0111:
 - Adding the rightmost two bits can be done with a half adder

$$\begin{array}{r} & 1 \\ 001\mathbf{1} & \\ + 011\mathbf{1} & \\ \hline & 0 \end{array}$$

Full Adder

- Why do they call it a half adder?
- To find the answer to this, we need to try to add two multi-bit numbers
- Let's add 0011 and 0111:
 - Adding the rightmost two bits can be done with a half adder
 - What about the next two bits?

$$\begin{array}{r} & 1 & 1 \\ & 00 & \mathbf{1}1 \\ + & 01 & \mathbf{1}1 \\ \hline & 10 & \end{array}$$


Full Adder

- Why do they call it a half adder?
- To find the answer to this, we need to try to add two multi-bit numbers
- Let's add 0011 and 0111:
 - Adding the rightmost two bits can be done with a half adder
 - What about the next two bits?
 - We really need to add three bits, in the general case
 - For this we need a new component: the full adder (FA)

$$\begin{array}{r} & 1 & 1 \\ & 00 & \mathbf{1}1 \\ + & 01 & \mathbf{1}1 \\ \hline & 10 & \end{array}$$


Full Adder

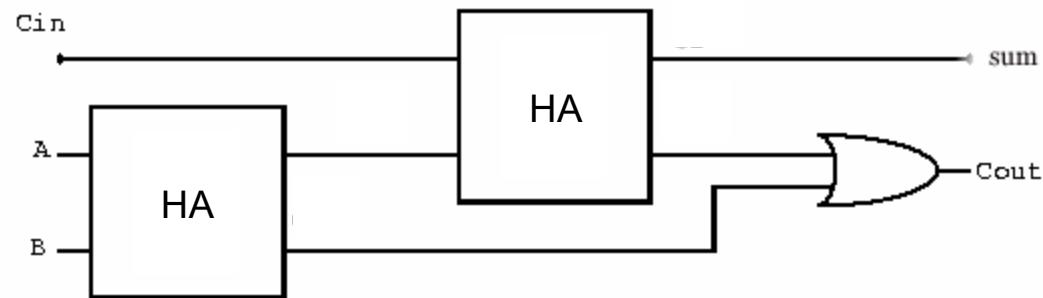- A full adder (FA) adds three bits
 - Inputs:
 - A and B: The bits to be added
 - C_{in} : A carry from a previous add, which also must be added
 - Outputs:
 - S: The sum of the three bits
 - C_{out} : Whether or not the sum resulted in a carry bit



Ripple Carry Adder

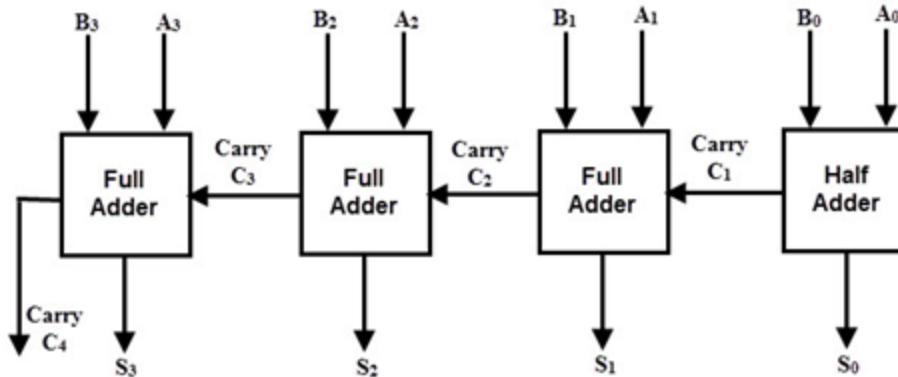- We could have drawn this entire circuit using XOR, AND, and OR gates
- This is our first circuit, drawn using block notation
- This is called a *ripple carry adder*



Fast Carry Adder

- A ripple carry adder requires that the carry propagates from one adder to the next
 - For a 64-bit adder, this would take 64 clock cycles
- A fast carry adder is exactly the same, but calculates the carry in inputs separately so that each full adder can determine its sum in the first clock cycle

Wrap-up

- Binary arithmetic
- Half adder
- Full adder
- Ripple carry adder
- Fast carry adder

What is next?

- Signed number representations
- Binary subtraction
- Overflow